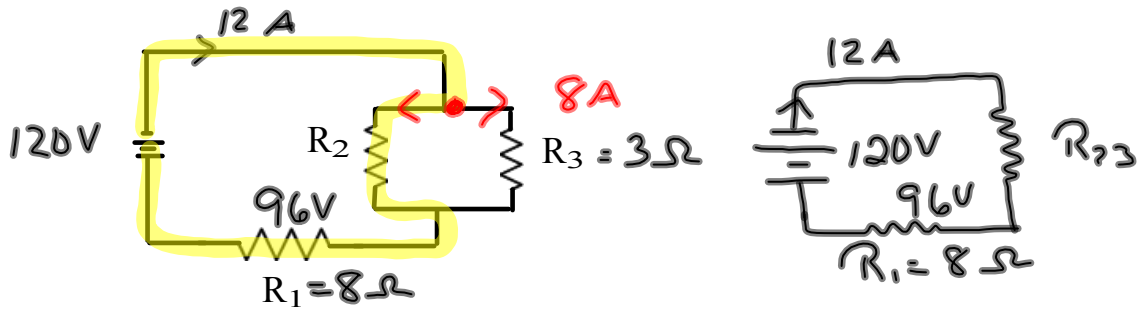


Section 10: Circuit Analysis II - Combination Circuits - Series - Parallel Circuits

1. An 8.0Ω (R_1) is connected in series with 2 resistors that are connected in parallel. One of the parallel resistors (R_3) has a resistance of 3.0Ω . The circuit is connected to a 120 V power supply and draws a total current of 12 A . Solve the circuit.



R1	8Ω	I1	12 A	V1	96 V
R2	6Ω	I2	4 A	V2	24 V
R3	3Ω	I3	8 A	V3	24 V
OPT. * R23		I23	12 A	V23	24 V
Rt	10Ω ✓	IT	12 A ✓	VT	120 V ✓

$$\textcircled{1} I_T = I_1 = I_{23} = 12 \text{ A}$$

$$\textcircled{2} R_T = \frac{V}{I} = \frac{120 \text{ V}}{12 \text{ A}} = 10 \Omega$$

$$\textcircled{3} V_1 = IR = (12 \text{ A})(8 \Omega) = 96 \text{ V}$$


$$\textcircled{4} V_{23} = V_T - V_1 = 120 \text{ V} - 96 \text{ V} = 24 \text{ V} = V_2 = V_3$$

$$\textcircled{5} I_3 = \frac{V}{R} = \frac{24 \text{ V}}{3 \Omega} = 8.0 \text{ A}$$

$$\textcircled{6} I_2 = I_T - I_3 = 12 \text{ A} - 8 \text{ A} = 4 \text{ A}$$

$$\textcircled{7} R_2 = \frac{V}{I} = \frac{24 \text{ V}}{4 \text{ A}} = 6.0 \Omega$$

2. Solve the circuit.

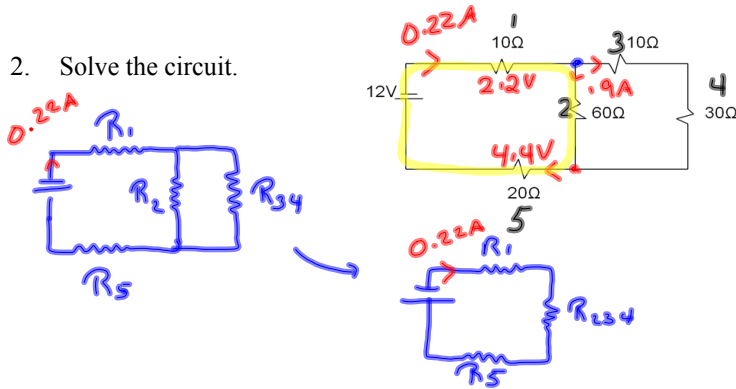

R1	10Ω	I1	0.22A	V1	2.2V
R2	60Ω	I2	0.09A	V2	5.4V
R3	10Ω	I3	0.13A	V3	1.3V
R4	30Ω	I4	0.13A	V4	3.9V
R5	20Ω	I5	0.22A	V5	4.4V
R34	40Ω	I34		V34	
R234	24Ω	I234		V234	
~~~~~					
Rt	54Ω	It	0.22A	Vt	12V

$$\textcircled{1} R_{34} = 10\Omega + 30\Omega = 40\Omega$$

$$\textcircled{2} \frac{1}{R_{234}} = \frac{1}{60\Omega} + \frac{1}{40\Omega}$$

$$R_{234} = 24\Omega$$

$$\textcircled{3} R_T = 10\Omega + 24\Omega + 20\Omega = 54\Omega$$

$$\textcircled{4} I_T = \frac{V_T}{R_T} = \frac{12V}{54\Omega} = 0.22A$$

$$\textcircled{5} I_T = I_1 = I_5 = 0.22A \quad (I_{234} = 0.22A)$$

$$\textcircled{6} V_1 = I_1 R_1 = (0.22A)(10\Omega) = 2.2V$$

$$\textcircled{7} V_5 = I R = (0.22A)(20\Omega) = 4.4V$$

$$V_{234} = I R = (0.22A)(24\Omega) = 5.3V$$

$$\textcircled{8} \text{KVL} \quad V_2 = V_T - V_1 - V_5 = 12V - 4.4V - 2.2V = 5.4V$$



$$\textcircled{9} I_2 = \frac{V}{R} = \frac{5.4V}{60\Omega} = 0.09A$$

$$\textcircled{10} \text{KCL} : I_{34} = I_T - I_2 = 0.22A - 0.09A = 0.13A = I_3 = I_4$$

$$\textcircled{11} V_3 = I R = 1.3V$$

$$V_4 = I R = 3.9V$$

3. Solve the circuit

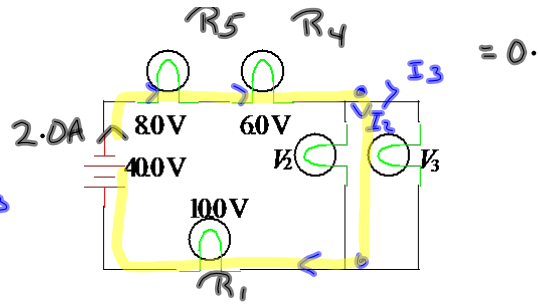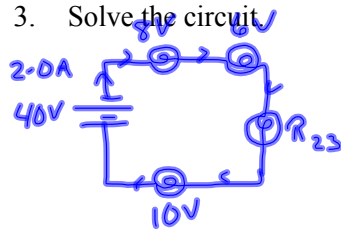

R ₁	5Ω	I ₁	2.0A	V ₁	10.0V
R ₂	10.7Ω	I ₂	1.5A	V ₂	16V
R ₃	32Ω	I ₃	0.5A	V ₃	16V
R ₄	3Ω	I ₄	2.0A	V ₄	6V
R ₅	4Ω	I ₅	2.0A	V ₅	8V
*R ₂₃	8Ω	I ₂₃	2.0A	V ₂₃	16V
R _T	20Ω	I _T	2.0A	V _T	40V

$$\textcircled{1} I_T = I_1 = I_4 = I_5 = (I_{23})$$

$$\textcircled{2} V_2 = V_T - V_1 - V_4 - V_5 = 40V - 8V - 6V - 10V = 16V = V_3$$

$$\textcircled{3} R_4 = \frac{V}{I} = \frac{6V}{2A} = 3\Omega$$

$$\textcircled{4} R_5 = \frac{8V}{2A} = 4\Omega$$

$$\textcircled{5} R_T = \frac{40V}{2A} = 20\Omega$$

$$\textcircled{6} R_1 = \frac{10V}{2A} = 5\Omega$$

$$\textcircled{7} R_{23} = \frac{16V}{2A} = 8\Omega$$

$$\textcircled{8} R_3 = \frac{V}{I} = \frac{16V}{0.5A} = 32\Omega$$

$$\textcircled{9} \frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{8\Omega} = \frac{1}{R_2} + \frac{1}{32\Omega}$$

$$\frac{1}{8\Omega} - \frac{1}{32\Omega} = \frac{1}{R_2}$$

$$10.7\Omega = R_2$$

$$\textcircled{10} I_2 = V_2 / R_2 = 16V / 10.7\Omega = 1.5A$$

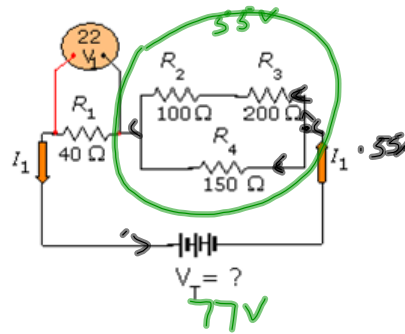4. The voltmeter in the circuit to the right measures a potential difference of 22 V across the 40 Ω resistor. Solve the circuit.



$R_1$	40 Ω	$I_1$	0.55 A	$V_1$	22 V
$R_2$	100 Ω	$I_2$	0.18 A	$V_2$	18 V
$R_3$	200 Ω	$I_3$	0.18 A	$V_3$	36 V
$R_4$	150 Ω	$I_4$	0.37 A	$V_4$	55 V
$\times R_{23}$	300 Ω	$I_{23}$	0.18 A	$V_{23}$	55 V
$* R_{234}$	100 Ω	$I_{234}$	0.55 A	$V_{234}$	55 V
$R_T$	140 Ω	$I_T$	0.55 A	$V_T$	77 V

$$\textcircled{1} R_{23} = 100 \Omega + 200 \Omega = 300 \Omega$$

$$\textcircled{2} \frac{1}{R_{234}} = \frac{1}{300 \Omega} + \frac{1}{150 \Omega}$$

$$R_{234} = 100 \Omega$$

$$\textcircled{3} R_T = 100 \Omega + 40 \Omega = 140 \Omega$$

$$\textcircled{4} I = \frac{V}{R} = \frac{22 \text{ V}}{40 \Omega} = 0.55 \text{ A}$$

$$\textcircled{5} I_T = I_1 = I_{234} = 0.55 \text{ A}$$

$$\textcircled{6} V_T = IR = (0.55 \text{ A})(140 \Omega) = 77 \text{ V}$$

$$V_{234} = (0.55 \text{ A})(100 \Omega) = 55 \text{ V}$$

$$V_{234} = 55 \text{ V} = V_4 = V_{23}$$


$$\textcircled{7} I_4 = \frac{V}{R} = \frac{55 \text{ V}}{150 \Omega} = 0.37 \text{ A}$$

$$\textcircled{8} I_{23} = \frac{V}{R} = \frac{55 \text{ V}}{300 \Omega} = 0.18 \text{ A} = I_2 = I_3$$

$$\textcircled{9} V_2 = IR = (0.18 \text{ A})(100 \Omega) = 18 \text{ V}$$

$$\textcircled{10} V_3 = IR = (0.18 \text{ A})(200 \Omega) = 36 \text{ V}$$

Ex.

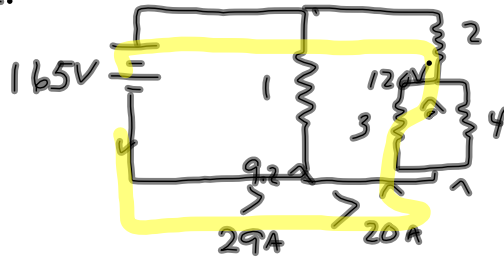

$$R_1 = 18\Omega$$

$$R_2 = 6.0\Omega$$

$$R_3 = 4.0\Omega$$

$$R_4 = 5.0\Omega$$

$R_1$	$18\Omega$	$I_1$	$9.2A$	$V_1$	$165V$
$R_2$	$6.0\Omega$	$I_2$	$20A$	$V_2$	$120V$
$R_3$	$4.0\Omega$	$I_3$	$11A$	$V_3$	$45V$
$R_4$	$5.0\Omega$	$I_4$	$9A$	$V_4$	$45V$
$R_{34}$	$2.2\Omega$	$I_{34}$	$9A$	$V_{34}$	$45V$
$R_{234}$	$8.2\Omega$	$I_{234}$	$20A$	$V_{234}$	$165V$
$R_T$	$5.6\Omega$	$I_T$	$29A$	$V_T$	$165V$

$$\textcircled{1} \frac{1}{R_{34}} = \frac{1}{4\Omega} + \frac{1}{5\Omega}$$

$$R_{34} = 2.2\Omega$$

$$\textcircled{2} R_{234} = R_2 + R_{34}$$

$$= 2.2\Omega + 6\Omega$$

$$= 8.2\Omega$$

$$\textcircled{3} \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_{234}}$$

$$\frac{1}{R_T} = \frac{1}{18\Omega} + \frac{1}{8.2\Omega}$$

$$R_T = 5.6\Omega$$

$$\textcircled{4} I_T = \frac{V_T}{R_T} = \frac{165V}{5.6\Omega} = 29A$$

⑤ KVL

$$V_T = V_1 = 165V$$

$$V_T = V_{234} = 165V$$

$$\textcircled{6} I_1 = \frac{V}{R} = \frac{165V}{18\Omega} = 9.2A$$

$$\textcircled{8} I_2 = 20A$$

$$\textcircled{7} I_{234} = \frac{V}{R} = \frac{165V}{8.2\Omega} = 20A$$


$$\textcircled{9} V_2 = IR = (20A)(6\Omega) = 120V$$

$$\textcircled{10} V_{34} = V_3 = V_4 = V_T - V_2 = 165V - 120V = 45V$$

$$\textcircled{11} I_3 = \frac{V}{R} = \frac{45V}{4\Omega} = 11A$$

$$I_4 = \frac{45V}{5\Omega} = 9A$$

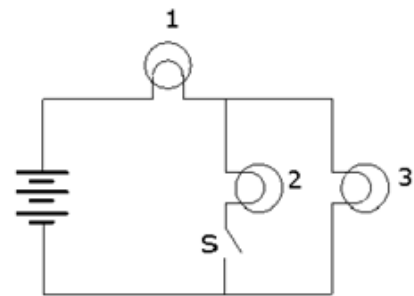5. The circuit below contains three identical light bulbs. Compare the brightness of bulb 1 and bulb 3 when switch, S, (i) is closed (ii) is opened.




When the switch is open, bulb 2 will not light. Bulb 1 and 3 will be in series and each will have the same brightness b/c each bulb will have the same voltage drop across it.

When the switch is close, all three bulbs will light. Bulb 2 and 3 are in parallel and their equivalent resistance is less than the individual resistance. This means that the total resistance of the circuit is decreased and therefor the total current of the circuit will increase. Hence the voltage drop across bulb 1 will be greater than before (bulb is brighter). As a result the current through Bulb 2 and 3 will be less. Therefore, bulb 3 will be less bright b/c of the smaller voltage drop across it.

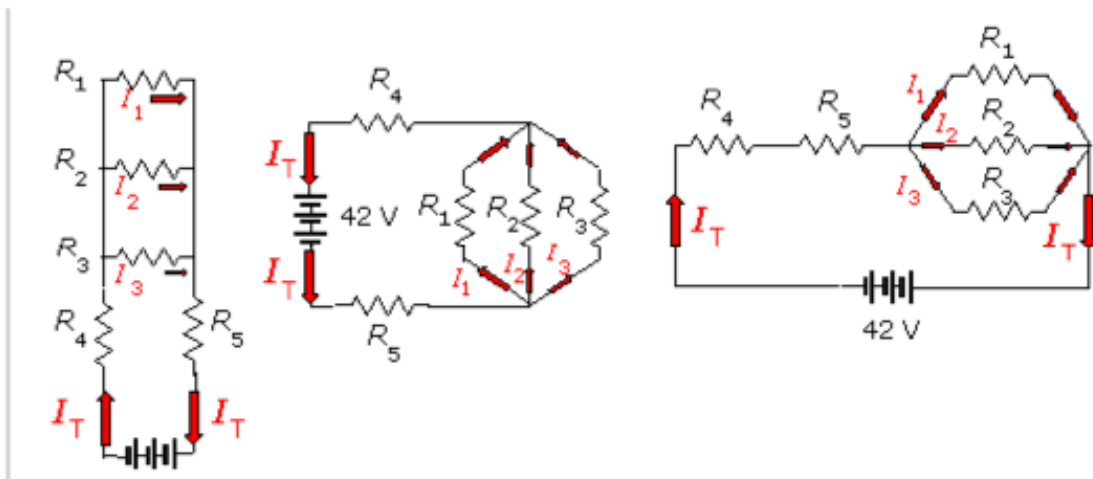6.  $R_1$ ,  $R_2$ , and  $R_3$  are connected in parallel and the combination is connected in series with  $R_4$  and  $R_5$ . Find the current through and the voltage drop across each of the resistors if the circuit has a 42 V source, and the values of the resistors are as follows:


$$R_1 = 75 \, \Omega \quad R_2 = 150 \, \Omega \quad R_3 = 120 \, \Omega \quad R_4 = 48 \, \Omega \quad R_5 = 36 \, \Omega$$



## Test yourself


1. Each resistor in the picture to the right has a resistance of  $15\ \Omega$ . What is the total resistance between points A and B?

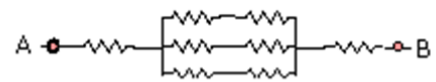- a)  $30\ \Omega$
- b)  $40\ \Omega$
- c)  $45\ \Omega$
- d)  $60\ \Omega$



2. Each resistance in the circuit to the right has a value of  $15\ \Omega$ . Which voltmeter will have the smallest reading?

- a) 1
- b) 2
- c) 3
- d) 4

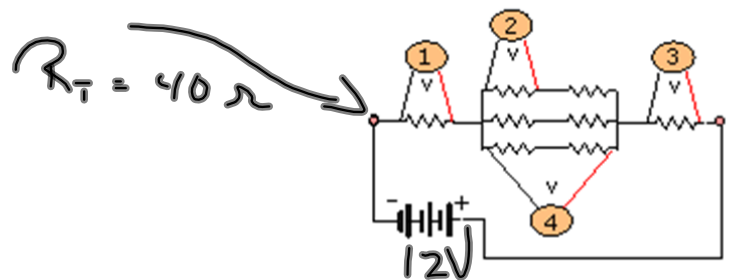




3. If the battery in the diagram of #2 is rated at 12.0 V, and if each resistor is 15  $\Omega$ , what current is the battery providing?

- a) 0.4 A
- b) 0.3 A
- c) 0.26 A
- d) 0.2 A


4. From the information in the circuit diagram to the right, what is the voltage of the battery?

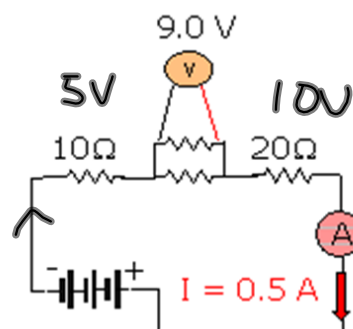- a) 9.0 V
- b) 33 V
- c) 19.5 V
- d) 24 V



5. An ammeter and a voltmeter are connected to two parallel branches as shown to the right. There is an opened switch in one of the branches. How will the readings on the ammeter and voltmeter be affected if the switch is closed?

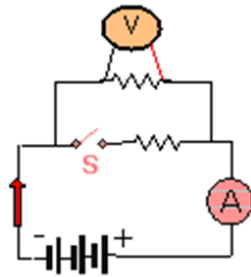- a) both V and A readings will increase
- b) the V reading will increase; the A reading will not change
- c) the A reading will increase; the V reading will not change
- d) both V and A readings will decrease



Handwritten notes in green ink:

$V = IR$

So  $V$  is same

↑

↓