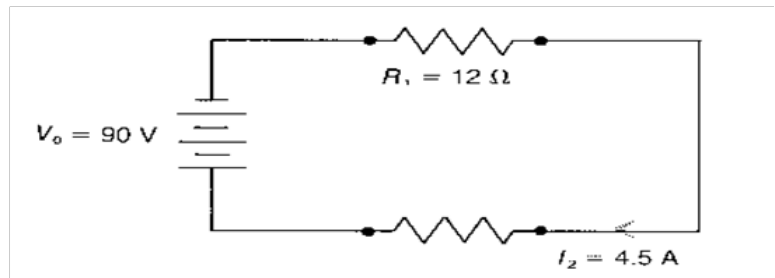


Section 10: Circuit Analysis I (Simple Series and Parallel Circuits)

1. Solve the circuit.



R_1	$12\ \Omega$	I_1	$4.5\ \text{A}$ ①	V_1	$54\ \text{V}$ ②
R_2	$8\ \Omega$ ④	I_2	$4.5\ \text{A}$	V_2	$36\ \text{V}$ ⑤
R_3	/	I_3	/	V_3	/
R_T	$20\ \Omega$ ③	I_T	$4.5\ \text{A}$ ①	V_T	$90\ \text{V}$

$$\textcircled{1} I_1 = I_2 = I_T = 4.5\ \text{A}$$


$$\textcircled{2} V_1 = IR = (4.5\ \text{A})(12\ \Omega) = 54\ \text{V}$$

$$\textcircled{3} R_T = \frac{V}{I} = \frac{90\ \text{V}}{4.5\ \text{A}} = 20\ \Omega$$

$$\textcircled{4} R_2 = R_T - R_1 = 20\ \Omega - 12\ \Omega = 8\ \Omega$$

$$\textcircled{5} V_2 = V_T - V_1 = 90\ \text{V} - 54\ \text{V} = 36\ \text{V}$$

2. Solve the circuit.

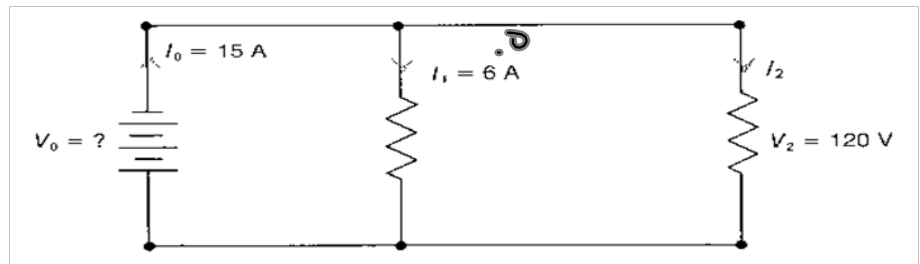

R_1	20Ω ④	I_1	$6A$	V_1	$120V$ ③
R_2	13Ω ②	I_2	$9A$ ①	V_2	$120V$
R_3	—	I_3	—	V_3	—
R_T	8Ω	I_T	$15A$	V_T	$120V$ ③

$$\textcircled{1} I_2 = 15A - 6A = 9A$$


$$\textcircled{2} R_2 = \frac{V_2}{I_2} = \frac{120V}{9A} = 13.3\Omega = 13\Omega$$

$$\textcircled{3} V_T = V_1 = V_2 = 120V$$

$$\textcircled{4} R_1 = \frac{V}{I} = \frac{120V}{6A} = 20\Omega$$

$$\textcircled{5} R_T = \frac{V}{I} = \frac{120V}{15A} = 8\Omega$$

3. Solve the circuit.

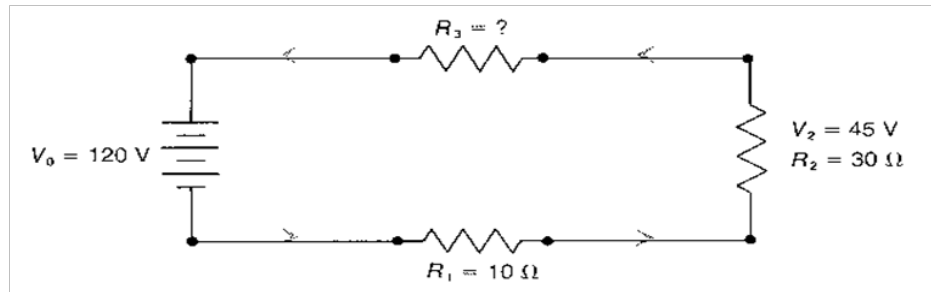

R_1	$10\ \Omega$	I_1	1.5 A	V_1	15 V
R_2	$30\ \Omega$	I_2	1.5 A	V_2	45 V
R_3	$40\ \Omega$	I_3	1.5 A	V_3	60 V
R_T	$80\ \Omega$	I_T	1.5 A	V_T	120 V

$$\textcircled{1} I_2 = \frac{V_2}{R_2} = \frac{45\text{ V}}{30\ \Omega} = 1.5\text{ A}$$

$$\textcircled{2} I_1 = I_2 = I_3 = I_T = 1.5\text{ A}$$


$$\textcircled{3} V_1 = IR: (1.5\text{ A})(10\ \Omega) = 15\text{ V}$$

$$\textcircled{4} R_T = \frac{V}{I} = \frac{120\text{ V}}{1.5\text{ A}} = 80\ \Omega$$

$$\textcircled{5} R_3 = 80\ \Omega - 10\ \Omega - 30\ \Omega = 40\ \Omega$$

$$\textcircled{6} V_3 = 120\text{ V} - 15\text{ V} - 45\text{ V} = 60\text{ V}$$

4. Solve the circuit.

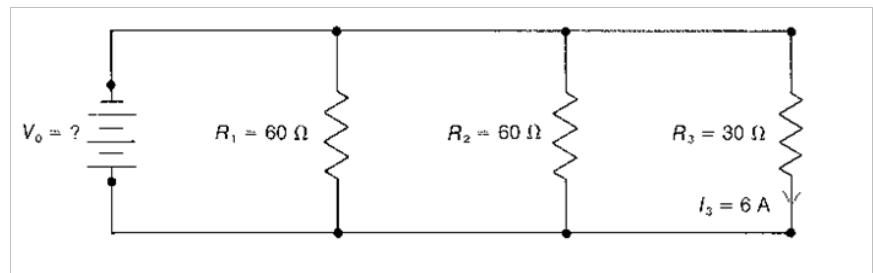

R_1	60Ω	I_1	3 A	V_1	180 V
R_2	60Ω	I_2	3 A	V_2	180 V
R_3	30Ω	I_3	6 A	V_3	180 V
R_T	15Ω	I_T	12 A	V_T	180 V

$$\textcircled{1} \quad \frac{1}{R_T} = \frac{1}{60 \Omega} + \frac{1}{60 \Omega} + \frac{1}{30 \Omega}$$

$$R_T = 15 \Omega$$

$$\textcircled{2} \quad V_3 = IR = (6 \text{ A})(30 \Omega) = 180 \text{ V}$$


$$\textcircled{3} \quad V_T = V_1 = V_2 = V_3 = 180 \text{ V}$$

$$\textcircled{4} \quad I_1 = \frac{V}{R} = \frac{180 \text{ V}}{60 \Omega} = 3 \text{ A}$$

$$\textcircled{5} \quad I_2 = \frac{180 \text{ V}}{60 \Omega} = 3 \text{ A}$$


$$\textcircled{6} \quad I_T = \frac{180 \text{ V}}{15 \Omega} = 12 \text{ A}$$

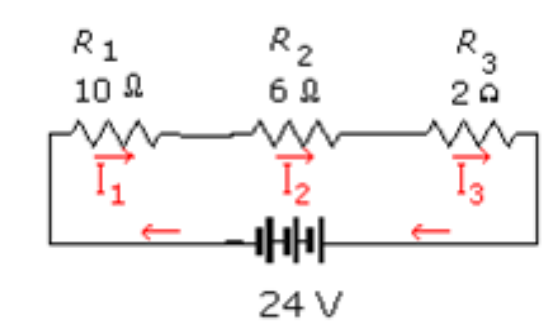5. Three resistors of 10.0Ω , 6.0Ω and 2.0Ω are connected in series across a 24 V battery. Find the current through and the voltage drop across each resistor.



R_1	10Ω	I_1	1.3 A	V_1	13 V
R_2	6Ω	I_2	1.3 A	V_2	7.8 V
R_3	2Ω	I_3	1.3 A	V_3	2.6 V
R_T	18Ω	I_T	1.3 A	V_T	24 V

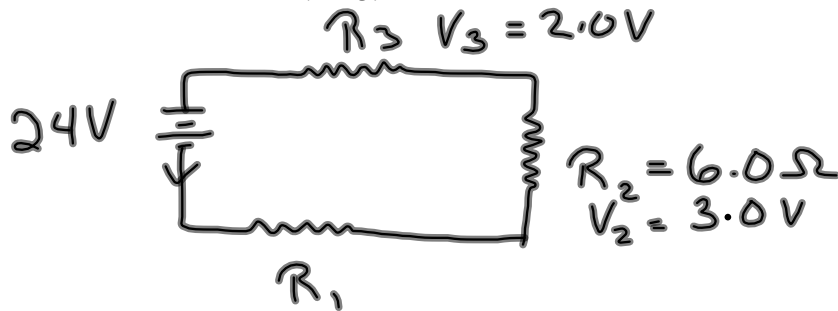6. Three resistors are connected in series. $R_2 = 6.0 \Omega$. The battery is 24 V and the voltage drop across resistor 2 is 3.0 V and the voltage drop across resistor 3 is 2.0 V. Draw a diagram of the circuit and find R_1 , R_3 , V_1 and I_1 .



R_1	38Ω	I_1	$0.50A$	V_1	$19V$
R_2	6.0Ω	I_2	$0.50A$	V_2	$3.0V$
R_3	4.0Ω	I_3	$0.50A$	V_3	$2.0V$
R_T	48Ω	I_T	$0.50A$	V_T	$24V$

$$\textcircled{1} V_1 = 24V - 3V - 2V = 19V$$

$$\textcircled{2} I_2 = \frac{V}{R} = \frac{3V}{6\Omega} = 0.50A$$


$$\textcircled{3} I_1 = I_2 = I_3 = I_T = 0.50A$$

$$\textcircled{4} R_1 = \frac{V}{I} = \frac{19V}{0.5A} = 38\Omega$$

$$\textcircled{5} R_3 = \frac{2V}{0.5A} = 4.0\Omega$$

$$\textcircled{6} R_T = \frac{24V}{0.5A} = 48\Omega$$

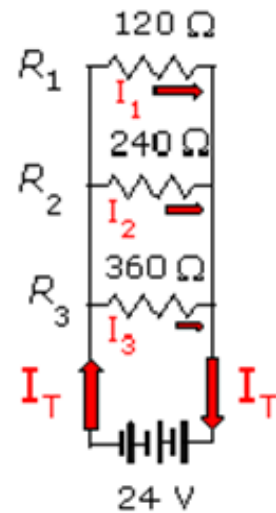7. A parallel combination of $120\ \Omega$, $240\ \Omega$, and $360\ \Omega$ is connected across a $24.0\ \text{V}$ power supply. Find the total current supplied by the battery.




R_1	$120\ \Omega$	I_1	$0.20\ \text{A}$	V_1	$24\ \text{V}$
R_2	$240\ \Omega$	I_2	$0.10\ \text{A}$	V_2	$24\ \text{V}$
R_3	$360\ \Omega$	I_3	$0.067\ \text{A}$	V_3	$24\ \text{V}$
R_T	$65\ \Omega$	I_T	$0.37\ \text{A}$	V_T	$24\ \text{V}$

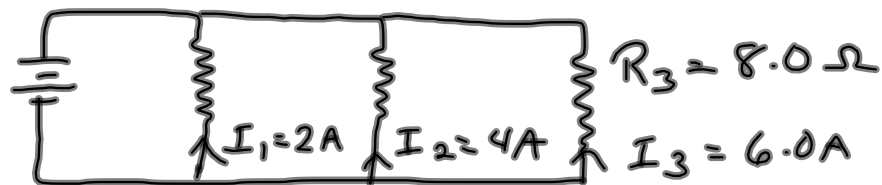8. Three resistors are connected in parallel

$$R_3 = 8.0\Omega, I_1 = 2.0A, I_2 = 4.0A, I_3 = 6A$$

Draw the circuit and find $V_T, V_1, I_T, R_1, R_2,$ and R_T



R_1	24Ω	I_1	$2A$	V_1	$48V$
R_2	12Ω	I_2	$4A$	V_2	$48V$
R_3	8Ω	I_3	$6A$	V_3	$48V$
R_T	4Ω	I_T	$12A$	V_T	$48V$

$$\textcircled{1} V_3 = IR = (6A)(8\Omega) = 48V$$

$$\textcircled{2} V_1 = V_2 = V_3 = V_T = 48V$$

$$\textcircled{3} I_T = 2A + 4A + 6A = 12A$$