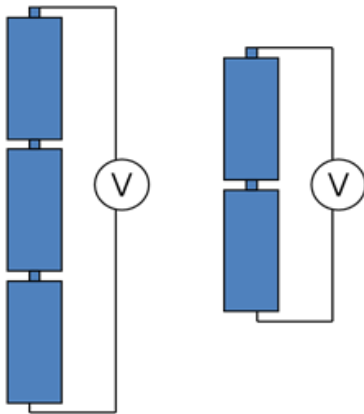


Section 5: Cells and Batteries


A combination of cells is called a **battery**. Cells are commonly combined so that they can generate a larger potential difference - the greater the number of cells, the stronger the battery and the more expensive the battery.

Cells in Series




$$V_T = V_1 + V_2 + \dots$$

Cells in Parallel

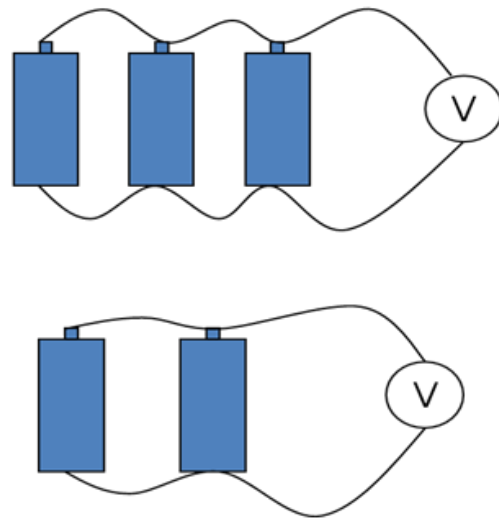

$$V_T = V_1 = V_2 = \dots$$

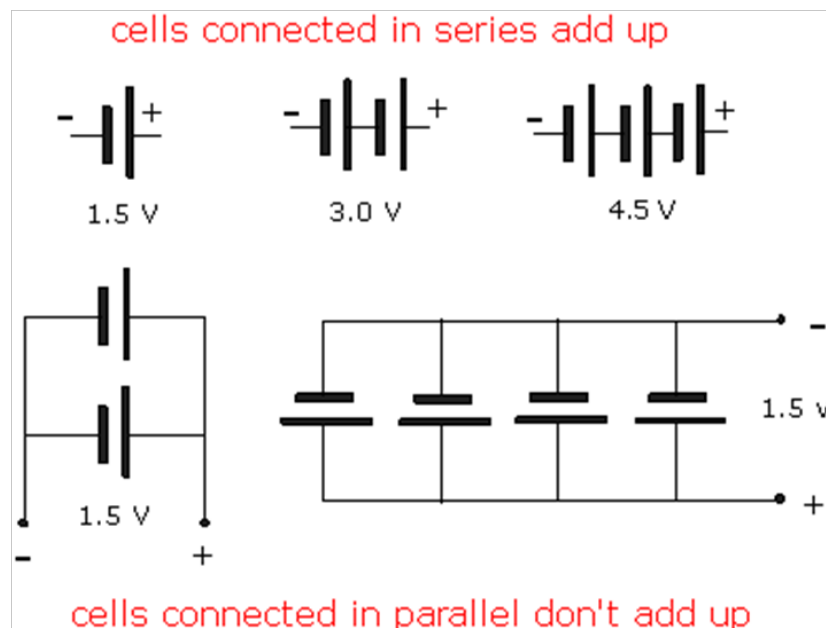

Question: If cells in parallel maintain the same voltage as a single cell, what's the point in using such arrangements?


Answer: Cells connected in parallel last longer. Each cell in parallel is providing only a portion of the required current. For example, if a current of one ampere is being drawn from four cells in parallel, then each cell provides only 1/4 of an ampere. This means the 4 cells will last 4 times longer than one cell.

The advantage of connecting cells in series is obvious: the resulting battery has a higher voltage than a single cell. (The larger the voltage, the larger the current that can be provided - - more on this later - Ohm's Law)

Examples:

- Find the voltage of each combination if the voltage of each cell is 1.5 V.


A)

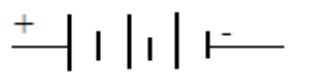


$$V_T = 3 \times 1.5 \text{ V}$$

$$= 4.5 \text{ V}$$

B)

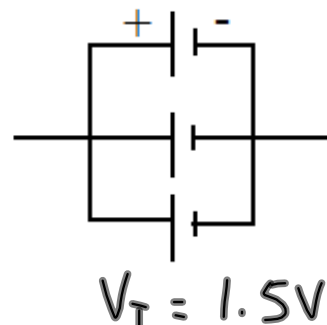

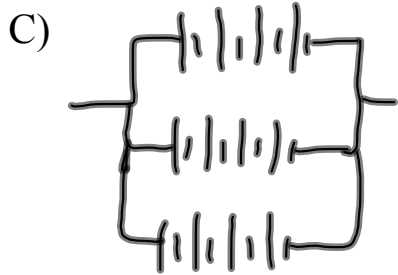

$$V_T = 4 \times 1.5 \text{ V} \\ = 6 \text{ V}$$

D)

2. The battery required by a CD player can provide 10 C of charge when the chemical action in the battery expends 90 J of energy. How many dry cells would it take to operate the CD player?

$$Q = 10 \text{ C} \\ E = 90 \text{ J}$$

$$V = \frac{E}{Q} = \frac{90 \text{ J}}{10 \text{ C}} = 9 \text{ V}$$

$$N = ?$$

$$9 \text{ V} \div 1.5 \text{ V} = 6 \text{ cells in series}$$

3. How many electrons move through a circuit when $3.0 \times 10^2 \text{ J}$ of energy are expended by two 1.5 V cells connected in series?

$$V = 3 \text{ V} \\ E = 300 \text{ J}$$

$$N = ?$$

$$Q = ?$$

$$V = \frac{E}{Q}$$

$$Q = \frac{E}{V} = \frac{300 \text{ J}}{3.0 \text{ V}} = 100 \text{ C}$$

$$Q = Ne$$

$$N = \frac{Q}{e} = \frac{100 \text{ C}}{1.602 \times 10^{-19} \text{ C}} = 6.2 \times 10^{20}$$