



Section 6: Introduction to Resistance

Recall:

Voltage or potential difference (V) may be thought of as the force behind the current (I). Thinking of voltage as a force suggests that the larger the voltage of a source, the more current will be pushed through the circuit. Large V means large I . **To make that last statement it is assumed that the resistance of the path doesn't change.**

To investigate the relation between the Voltage (or Potential Difference) and the rate of current flow, we can apply different potentials across a toaster element, a resistor, and monitor the corresponding currents that result.

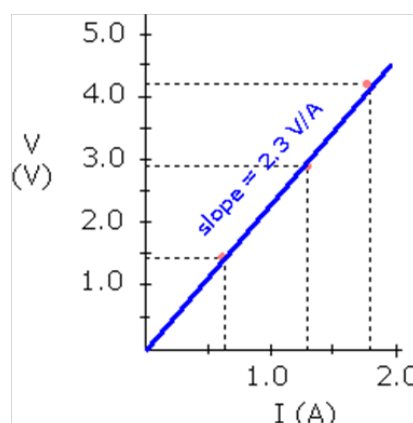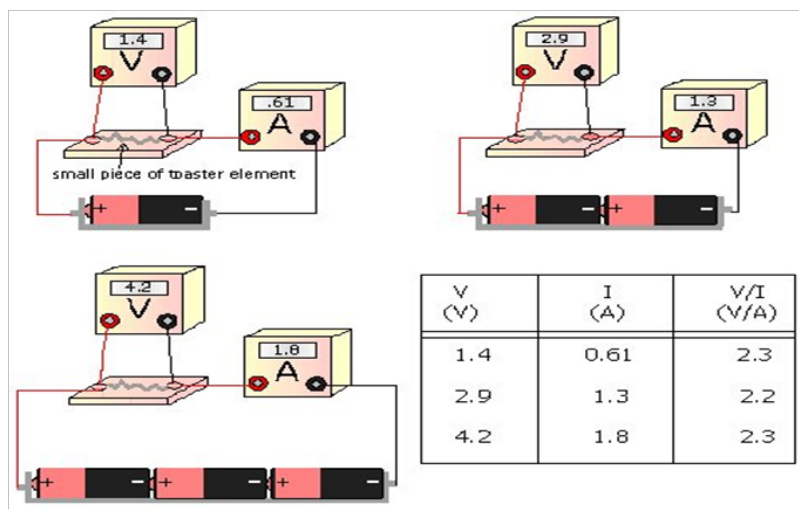The picture below shows 3 circuits. One, two and three 1.5 V cells are connected in series with a small piece of toaster element mounted on a piece of wood. An ammeter and a voltmeter give the current and voltage readings for each set-up. These measurements are also tabulated in the accompanying table.



$$V \propto I$$

Note that V vs. I is a straight line which means that for this particular circuit element the ratio of potential difference to the current is constant. This **ratio** (which can be found by calculating the slope) is referred to as the **resistance**. The **slope** or **resistance of this element** is 2.3 V/A or 2.3Ω .

The SI unit of resistance is the ohm and uses the Greek symbol omega, " Ω ".

A resistance of 1Ω means that a potential difference of 1 V applied across the ends of the device will sustain a current of 1 ampere . 10Ω of resistance means that a potential difference of 10 V is necessary to sustain a current of 1 A .

This is Ohm's Law, $R = \frac{V}{I}$ $\frac{V}{A} = \frac{J/C}{C/S} = \frac{J \times S}{C^2} = \frac{J \cdot s}{C^2}$

where: **R** is called the resistance in ohms (Ω) and it depends on the particular conductor. $1 \Omega = 1 \text{ V} / 1 \text{ A}$

V is the potential difference in volts (**V**)


I is the current in amperes (**A**)

Ohm's Law:


The current in a circuit is directly proportional to the voltage applied as long as the resistance in the circuit does not change.

A **linear** or **ohmic resistor** is one for which the graph of Voltage (**V**) versus Current (**I**) is a straight line. The slope of the line is the resistance; the greater the slope, the greater the resistance.


A has the greater resistance.

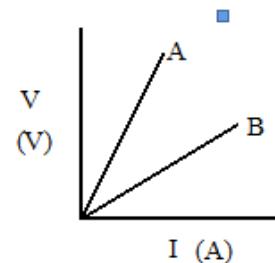

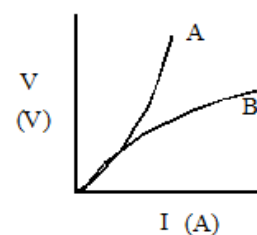
A **non-linear** or **non-ohmic** resistor is one for which the graph of Voltage (**V**) versus Current (**I**) is a curve.



Non-ohmic Circuit Elements

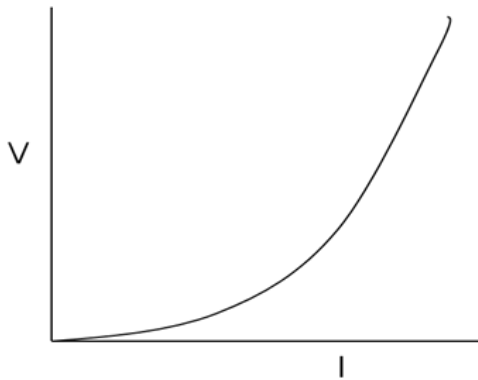

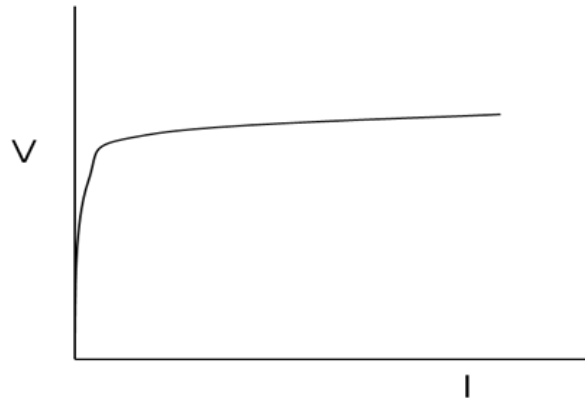This graph is typical of a light bulb. Resistance increases as the filament heats up.



This graph is typical of a diode, a semiconductor. Under lower voltages it behaves very much like an insulator. Then, when the voltage is right it "cuts in" and acts conductor!

Rearrangements of the Formula: $R = \frac{V}{I}$

$$\boxed{V = IR}$$

$$V \propto I, \text{ if } R \text{ is constant } \checkmark$$

$$V \propto R, \text{ if } I \text{ is constant}$$

$$I \propto \frac{1}{R} \text{ if } V \text{ is constant } \checkmark$$

Examples:

1. A 30 V battery maintains current through a $10\ \Omega$ resistor. What is the current?

$$R = \frac{V}{I}$$

$$I = \frac{V}{R} = \frac{30\text{V}}{10\ \Omega} = 3\text{A}$$

2. A 12 V battery is connected to a device and 24 mA of current flows through it. If the device obeys Ohm's Law, how much current will flow when a 24 V battery is used?

$$V_1 = 12\text{ V} \quad V_2 = 24\text{ V}$$

$$I_1 = 24\text{ mA} \quad I_2 = ?$$

$$R = ? \quad \text{Same}$$

①

* Ohm's Law states $V \propto I$ if R is constant
 \therefore if V is doubled, I is doubled
 $\therefore I = 48\text{ mA}$


② If the device obeys Ohm's Law, then R is constant. So, we can find R first.

3. An FRS radio is operated by 4 AA cells. If the device has a resistance of $26.8\ \Omega$, what current does the device draw?

Test yourself


1. The graph below results when a variable voltage source is placed across a substance of unknown resistance and the current is measured for different applied voltages. What is value of the resistance?

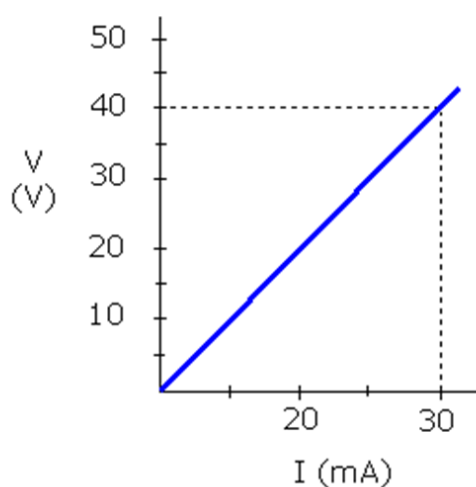- a) 1.3Ω
- b) 0.75Ω
- c) 1300Ω
- d) 750Ω



2. Which is the most sensible statement regarding the graph below?

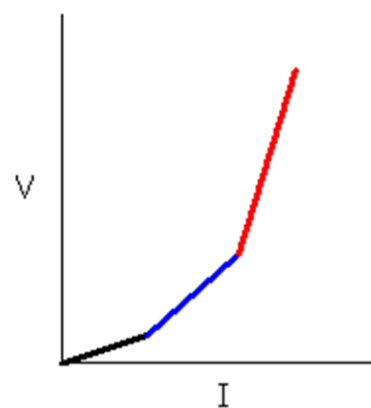- a) 3 different voltages were applied
- b) the resistance in the circuit became larger as the current increased
- c) the resistance in the circuit has an infinite number of values
- d) three different currents were measured



3. Which of the following is not an expression of Ohm's Law?

- a) $I = R/V$
- b) $V = IR$
- c) $V = RI$
- d) $R = V/I$

4. In a certain circuit $V = v$, $I = i$ and $R = r$. What will be the value of the current if the voltage is doubled and the resistance tripled?

- a) i
- b) $(2/3) i$
- c) $(3/2) i$
- d) $3v/2r$